

anish kushwaha

B.R.

EE-101/1846

B. Tech. (Semester-I) Exam.- 2012
Electrical Engg.

Time: Three Hours
Maximum Marks: 100

①
Solving.

Note: Attempt question from all the sections.

Section -A

(Short Answer Type Questions)

Note: Attempt any ten questions. Each question carries four marks. (4x10=40)

Q.1.


State and explain Kirchhoff's laws with suitable examples.

Q.2.

State and explain super position theorem. Mention its limitations.

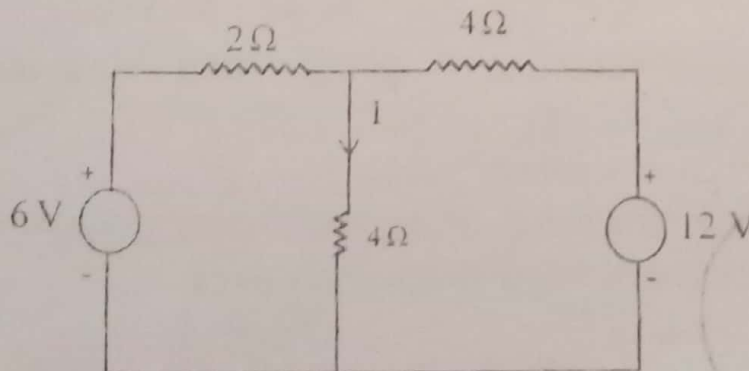Q.3.

Find the current I using Thevenin's theorem in the network shown.



EE-101/1846-M-420


- 2/4. Explain the loop current method of solving a network.
- 10/4 5. Derive an expression for average and rms value of a sinusoidally varying a.c. voltage. P
- 6/6. Differentiate between form factor and peak factor. P
- 3/3 7. Explain the difference between apparent power, real power and reactive power. O
- 19/3 8. State the advantages of three phase system over single phase system.
- 8/9. Differentiate between recording and integrating type of instruments.
- 8/10. Explain magnetic and electric circuits. Give analogy between them.
11. State and explain Faraday's law of electromagnetic induction.
12. Explain the concept of mutual induction. Define coefficient of Coupling.
- 8/13. Explain the basic principle of operation of a single phase transformer. P
- 27/6 14. What is all-day efficiency of a transformer? How does it differ from ordinary efficiency?
- 8/15. Derive emf equation of a d.c. generator.

Section -B

(Long Answer Type Questions)

Note: Attempt any three questions. Each question carries twenty marks. (20x3=60)

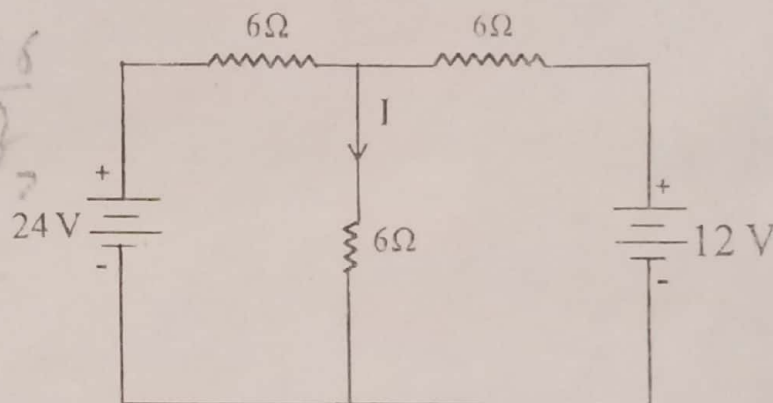1. (a) State and prove Thevenin's theorem. ✓
 P (b) Using super position theorem find the Current I in the network shown.



2. The equation of an alternating current $i = 42.42 \sin 628t$. Determine-
- (i) Its maximum value
 - (ii) Frequency
 - (iii) rms value
 - (iv) Average value
 - (v) Form factor
3. Explain the principle, construction and working of a PMMC type instrument. What will it give as an output if a half wave rectified a.c having peak value of 100 is given as input?

4. (a) ✓
p What is an auto-transformer? How does it differ from conventional two winding transformer? State its application.

(b) An auto-transformer is used to step down voltage level from 230 V to 200 V while the load is 20 KW at up f. Neglecting losses and magnetizing current. Find the current in different sections of the Winding.

5. ✓
p Explain the principle of operation and construction of a three phase induction motor. Hence, derive an expression for the frequency of rotor current in it.

6. (a) A coil of 300 turns, wound on a core of non-magnetic material, has an inductance of 10 m h. Calculate (i) the flux produced by a current of 5 A and (ii) the average value of emf induced when a current of 5 A is reversed in 8 milliseconds.

- (b) Explain the working principle of synchronous motor. Draw V-Curves and give its applications.