

~~13~~ EC-1869

B. Tech. (Semester-II) Examination 1998
Electronics Engg.

Time: Three Hours

Maximum Marks: 100

Note: Attempt questions from all the sections.

Section-A

(Short Answer Type Questions)


Note: Attempt any ten questions. Each question carries 10 marks.

(4x10=40)

~~Q1~~ Explain Semicconductors.

~~Q2~~ What is PN junction Diode? Sketch the characteristics of Si and Ge diodes.

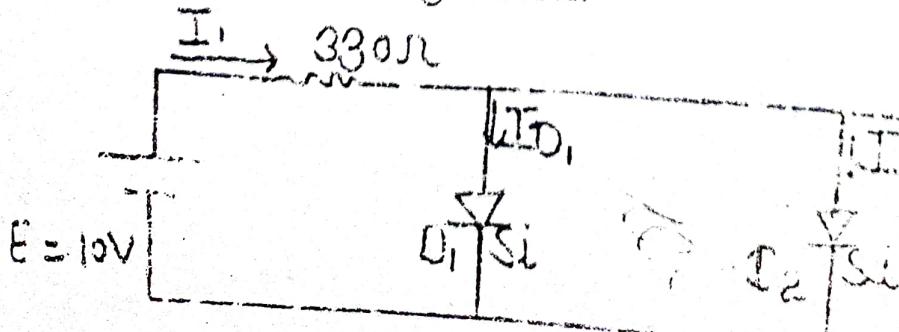3. Determine V_0 , I_1 , ID_1 and $n(D_1)$ for following diode configuration:-




20

2

Define PIV. Also write the different values of PIV for different rectifiers.

$$\text{PIV} = V_{m2}$$

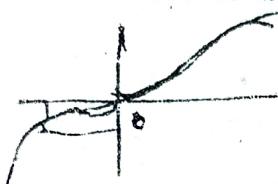What is zener diode? Sketch the $V - I$ characteristics of zener diode:



Draw the $V - I$ characteristics of CB transistor.

Compare the CB, CE and CC transistor configurations.

Design a fixed bias circuit using a silicon transistor having $\beta = 100$. V_{ce} is 10v and dc bias conditions are to be $V_{ce} = 5v$ and $I_c = 5mA$.

Differentiate between BJT and FET

~~NMOS~~

Write the important characteristics of an ideal operational amplifier.

Convert the following:

(a) $(0.625)_{10} = (?)_2$

(b) $(172.878)_{10} = (?)_8$

(c) $(ABC.75)_{16} = (?)_{10}$

(d) $(434.67)_8 = (?)_{16}$

$$(101112.75)_{16} = (?)_{10}$$

(a) 1.011 (b) 0.1010

13. Apply DeMorgan's theorem and simplify

$$\overline{A + BC} + D(\overline{E} + \overline{F})$$

14. Construct EX-OR gate using NAND gates only.

15. Simplify $\bar{A}BC + B\bar{C} + AB\bar{C} + A\bar{B}C$ using K-map.

Section-B

(Long Answer Type Questions)

Note: Attempt any three questions. Each question carries 20 marks. $(20 \times 3 = 60)$

1. Draw the circuit diagram of an OP-Amp as an adder, subtractor, differentiator and integrator. Then determine the output voltage for all the four configurations.

2. Draw the h-parameter equivalent of CE transistor and determine R_i , R_o , A_i and A_v expressions.

3. Draw the circuit diagram of an OP-Amp as an adder, subtractor, differentiator and integrator. Then determine the output voltage for all the four configurations.

- Q) (i) Describe the circuit diagram and input-output waveform for bridge (full wave) rectifier.
- (ii) Describe the shunt voltage filter used [circuit diagram].
- Q) Draw the circuit diagram and explain the working of
(i) Half wave voltage doubler circuit and
(ii) Full wave voltage doubler circuit

Explain the following:

- (i) FET 
- (ii) Zener breakdown 
- (iii) CMRR 
- (iv) Zener diode as shunt regulator 