

EC-1862
B.Tech.(Semester-II) Exam-2018
Electronics Engg.

Time: Three Hours
Maximum Marks: 100

Note: Attempt questions from all the sections.

Section-A

(Short Answer Type Questions)

Note: Attempt any ten questions. Each question carries 4 marks. (4x10=40)

1. Simplify the following Boolean Expression:

$$Y = \overline{BC} + \overline{AD}(\overline{AB} + \overline{CD})$$


$$Y = ABC + \overline{A}\overline{B}C + A\overline{B}\overline{C}$$

2. Explain how electrons are focused to a fine point on the screen of a CRT?

3. Explain how the V-I characteristic of p-n diode depend on temperature.

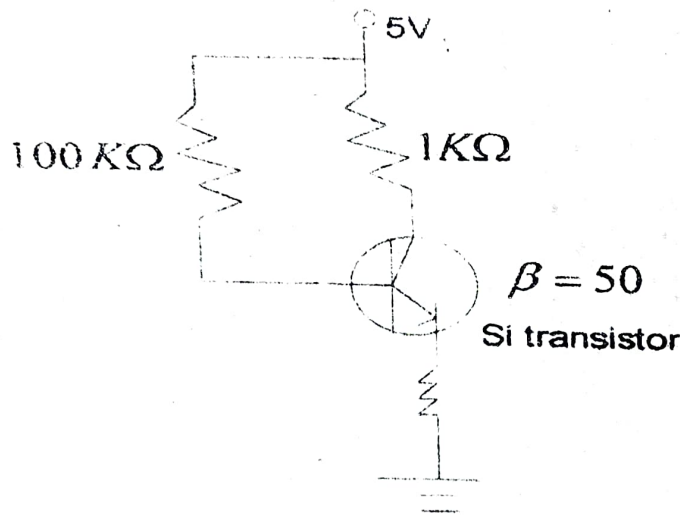4. Distinguish between p-type and n-type semiconductor with energy band diagram.

Draw the dc load line and determine the operation point.



6. List the characteristic of an ideal op-Amp.
7. For a transistor working in CB configuration explain the input and o/p characteristic with diagram.
8. Explain the working of full wave bridge rectifier with circuit diagram.
9. Explain how an op-Amp can be used as inverting amplifier with circuit diagram.
10. Differentiate between avalanche and zener breakdown.

11. How the dynamic resistance r of a pn-junction diode vary with (i) Current (ii) Temperature

12. What is advantage of FET over a bipolar junction transistor?

13. Convert the following:

(i) $(4021.25)_{10} = (---)$

(ii) $(A6F.CD)_{16} = (---)_8$

14. Explain the term:

(i) Input offset current

(ii) Slow rate

15. Explain:

(i) Potential barrier

(ii) Depletion layer

Section -B

(Long Answer Type Questions)

Note: Attempt any three questions. Each question carries 20 marks. (20x3=60)

1. Explain working of op-Amp as an inverting and non inverting amplifier.

2. (a) Convert the following number:
 - (i) $(1001)_8 = (---)_2$
 - (ii) $(2CCD)_{16} = ()_5$
 - (iii) $(.45)_{10} = ()_8$
 - (iv) $(345)_8 = ()_{10}$
 - (v) $(25)_x = (85)_{10}$ find x.
 (b) Write demorgan's theorem and canonical form of Boolean function.

3. A junction transistor has following parallel meter
 $h_{ie} = 2K$, $h_{re} = 1.6 \times 10^{-4}$, $h_{fe} = 50$
 $h_{oe} = 50 \mu A/V$. Determine (i) A_i, A_v, R_i, R_o of CE amplifier if load resistance is $12k\Omega$ and $R_s = 500\Omega$.

4. Differentiate between clipping and clamping with circuit diagram.

5. (a) Determine the Boolean function using k-map
 $f(ABCD) = \sum m(3,4,5,7,9,13,14,15) + d(0,2,8)$
 (b) Explain voltage full wave doubles with diagram.

6. (a) Explain the working principle of a CRO. Also writes its various applications.
 (b) Explain working of half wave rectifier circuit.

EC-1848

B.Tech. (Semester-I) Examination–2018 Electronics Engineering

Time: Three Hours

Maximum Marks: 100

Note: Attempt questions from all the sections.

Section-A

(Short Answer Type Questions)

Note: Attempt any ten questions. Each question carries equal marks. (4x10=40)

1. Explain with Circuit diagram full wave voltage doubles.
2. Sketch the circuit diagram of positive series clipper show in the i/p and o/p wave form.
3. What is Zener breakdown? Explain.
4. A certain transistor has $\beta=100$ if $I_C=50\text{ mA}$ find I_B .
5. Why an ordinary junction transistor is called bipolar.
6. Differentiate b/w clipper and clamper circuit.


7. Convert the following:
 - (a) $(1001)_8 = ()_2$
 - (b) $(.45)_{10} = ()_8$
 - (c) $(2CC^D)_{16} = ()_5$
8. Explain non inverting amplifier.
9. Define Canonical form of Boolean algebra. Define SOP and POS form.
10. Differentiate b/w depletion type and Enhancement type MOSFET.
11. Write the characteristics of ideal op-amp.
12. Define Shunt. Capacitor filter with circuit diagram.
13. Sketch the logic circuit for Boolean expressions
 - (a) $(\bar{A} + \bar{B}).C$
 - (b) $\bar{A}B + \bar{C}$
14. Explain the working of Zener diode as shunt regulator.
15. Define load regulation.

Section-B

(Long Answer Type Questions)

Note: Attempt any three questions. Each question carries 20 marks. (20x3=60)

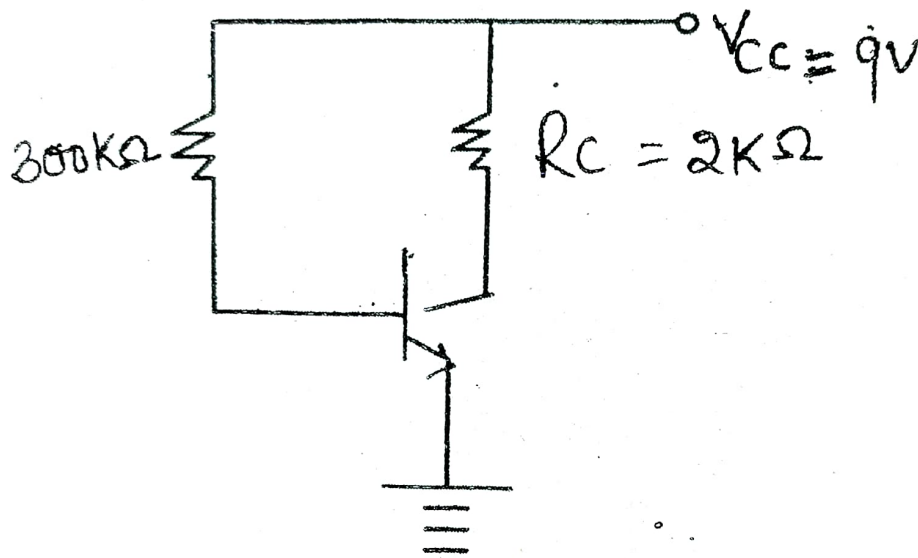1. (a) Find the Collector current and V_{CE} voltage for given circuit.



- (b) Convert the number $(306)_6$ to its Equivalent decimal number.
2. A transistor connected in CE configuration has $h_{ie} = 1k\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 2545$ and $r_s = r_L = 1k\Omega$. Calculate A_i , R_i , A_v , A_{is} , A_{vs} .
3. (a) Explain the working of CRO with block diagram.

(b) Simplify the following expression

(a) $Y = ABC\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{C}\bar{B} + A\bar{B}$


(b) $Y = (A + BC)(D + EF)$

4. (a) Simplify using K-map

$W(A, B, C, D) \Sigma M(0, 2, 6, 11, 13, 14)$

(b) Explain the working of op-amp as adder.

5. Write expression of X

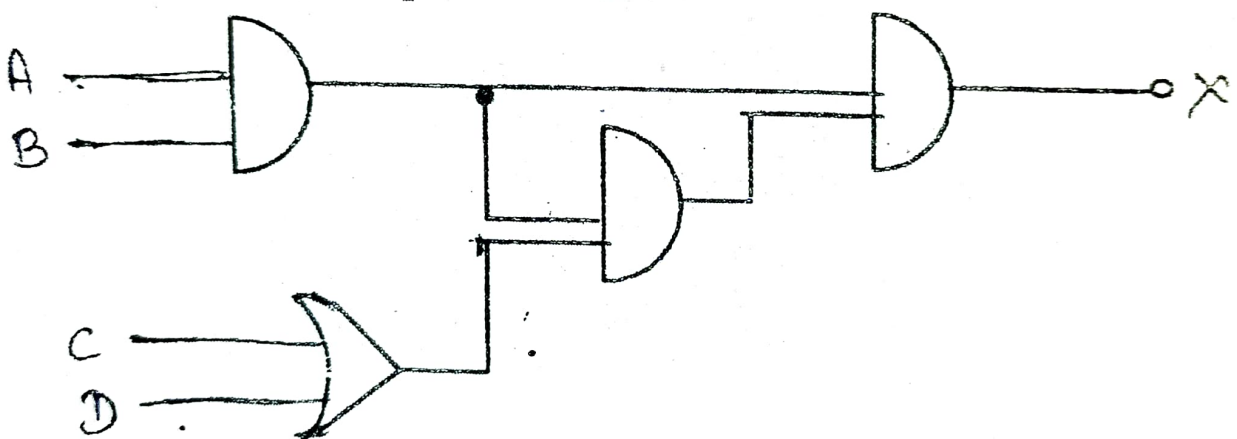

(b) With Construction diagram explain the working of P-CH depletion type MOSFET.

6. A self biased FET amplifier circuit has $R_G = 2\text{m}\Omega$, $R_D = 2.7\text{K}\Omega$ and $R_S = 1\text{K}\Omega$. Computes V_{GS} , I_D and V_{DS} . If the FET has $I_{DSS} = 3\text{mA}$ and $V_p = 2.4\text{V}$.